

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dff is
    port(    D: in STD_LOGIC;
            Q: out STD_LOGIC;
            Clock: in STD_LOGIC;
            Clear: in STD_LOGIC);
end dff;

architecture Behavioral of dff is
begin
    process(Clock) --eğer clock değişirse alttaki begin-end process i çalıştır --
    begin
        if(rising_edge(Clock)) then
            if(Clear='0') then
                Q <= '0';
                --Qn <= '1';

            else
                Q <= D;
                --Qn <= not(D);
            end if;
        end if;
    end process;
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux4x1 is
    port( A,B,C,D : in STD_LOGIC;
          S0,S1: in STD_LOGIC;
          Z: out STD_LOGIC );

```

```
end mux4x1;
```

architecture Behavioral of mux4x1 is

```
begin
```

```
process(A,B,C,D,S0,S1) is
```

```
begin
```

```
    if(S1='0' and S0='0') then
```

```
        Z<=A;
```

```
    elsif(S1='0' and S0='1') then
```

```
        Z<=B;
```

```
    elsif(S1='1' and S0='0') then
```

```
        Z<=C;
```

```
    else
```

```
        Z<=D;
```

```
    end if;
```

```
end process;
```

```
end Behavioral;
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity dff_and_mux is
```

```
    port( dff_mux_4: in STD_LOGIC_VECTOR (3 downto 0);
```

```
          serial_shift_2: in STD_LOGIC_VECTOR (1 downto 0);
```

```
          Clk: in STD_LOGIC;
```

```
          Clr: in STD_LOGIC;
```

```
          Q_out: out STD_LOGIC);
```

```
end dff_and_mux;
```

architecture Behavioral of dff_and_mux is

component mux4x1 is

```
port( A,B,C,D : in STD_LOGIC;
      S0,S1: in STD_LOGIC;
      Z: out STD_LOGIC );
```

end component;

component dff is

```
port( Q: out STD_LOGIC;
      --Qn: out STD_LOGIC;
      Clock: in STD_LOGIC;
      Clear: in STD_LOGIC;
      D: in STD_LOGIC);
```

end component;

signal mux_to_dff: STD_LOGIC;

begin

```
B1: mux4x1 port map( A=>dff_mux_4(0),
                    B=>dff_mux_4(1),
                    C=>dff_mux_4(2),
                    D=>dff_mux_4(3),
                    S0=>serial_shift_2(0),
                    S1=>serial_shift_2(1),
                    Z=>mux_to_dff);
```

```
B2: dff port map( Q=>Q_out,
                  Clock=>Clk,
                  Clear=>Clr,
                  D=>mux_to_dff);
```

end Behavioral;

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity odev4 is
```

```
    port( I_4: in STD_LOGIC_VECTOR (3 downto 0);
```

```
          SSR: in STD_LOGIC; --serial input for shift right
```

```
          SSL: in STD_LOGIC; --serial input for shift left
```

```
          S1_sr: in STD_LOGIC;
```

```
          S0_sr: in STD_LOGIC;
```

```
          Clock_sr: in STD_LOGIC;
```

```
          Clear_sr: in STD_LOGIC;
```

```
          A_4: out STD_LOGIC_VECTOR (3 downto 0));
```

```
end odev4;
```

```
architecture Behavioral of odev4 is
```

```
    component dff_and_mux is
```

```
        port( dff_mux_4: in STD_LOGIC_VECTOR (3 downto 0);
```

```
              serial_shift_2: in STD_LOGIC_VECTOR (1 downto 0);
```

```
              Clk: in STD_LOGIC;
```

```
              Clr: in STD_LOGIC;
```

```
              Q_out: out STD_LOGIC);
```

```
    end component;
```

```
    signal store_4: STD_LOGIC_VECTOR (3 downto 0);
```

```
    signal shift_right: STD_LOGIC_VECTOR (3 downto 0);
```

```
    signal shift_left: STD_LOGIC_VECTOR (2 downto 0);
```

```
begin
```

```
    B1: dff_and_mux port map(dff_mux_4(0)=>store_4(3),
```

```
dff_mux_4(1)=>SSR,  
dff_mux_4(2)=>shift_left(2),  
dff_mux_4(3)=>l_4(3),  
serial_shift_2(0)=>S0_sr,  
serial_shift_2(1)=>S1_sr,  
Clk=>Clock_sr,  
Clr=>Clear_sr,  
Q_out=>shift_right(3));
```

```
B2: dff_and_mux port map(dff_mux_4(0)=>store_4(2),  
    dff_mux_4(1)=>shift_right(3),  
    dff_mux_4(2)=>shift_left(1),  
    dff_mux_4(3)=>l_4(2),  
    serial_shift_2(0)=>S0_sr,  
    serial_shift_2(1)=>S1_sr,  
    Clk=>Clock_sr,  
    Clr=>Clear_sr,  
    Q_out=>shift_right(2));
```

```
B3: dff_and_mux port map(dff_mux_4(0)=>store_4(1),  
    dff_mux_4(1)=>shift_right(2),  
    dff_mux_4(2)=>shift_left(0),  
    dff_mux_4(3)=>l_4(1),  
    serial_shift_2(0)=>S0_sr,  
    serial_shift_2(1)=>S1_sr,  
    Clk=>Clock_sr,  
    Clr=>Clear_sr,  
    Q_out=>shift_right(1));
```

```
B4: dff_and_mux port map(dff_mux_4(0)=>store_4(0),  
                        dff_mux_4(1)=>shift_right(1),  
                        dff_mux_4(2)=>SSL,  
                        dff_mux_4(3)=>I_4(0),  
                        serial_shift_2(0)=>S0_sr,  
                        serial_shift_2(1)=>S1_sr,  
                        Clk=>Clock_sr,  
                        Clr=>Clear_sr,  
                        Q_out=>shift_right(0));
```



```
A_4(3)<=shift_right(3);  
store_4(3)<=shift_right(3);
```



```
A_4(2)<=shift_right(2);  
store_4(2)<=shift_right(2);  
shift_left(2)<=shift_right(2);
```


```
A_4(1)<=shift_right(1);  
store_4(1)<=shift_right(1);  
shift_left(1)<=shift_right(1);
```

```
A_4(0)<=shift_right(0);  
store_4(0)<=shift_right(0);  
shift_left(0)<=shift_right(0);
```

```
end Behavioral;
```

  

 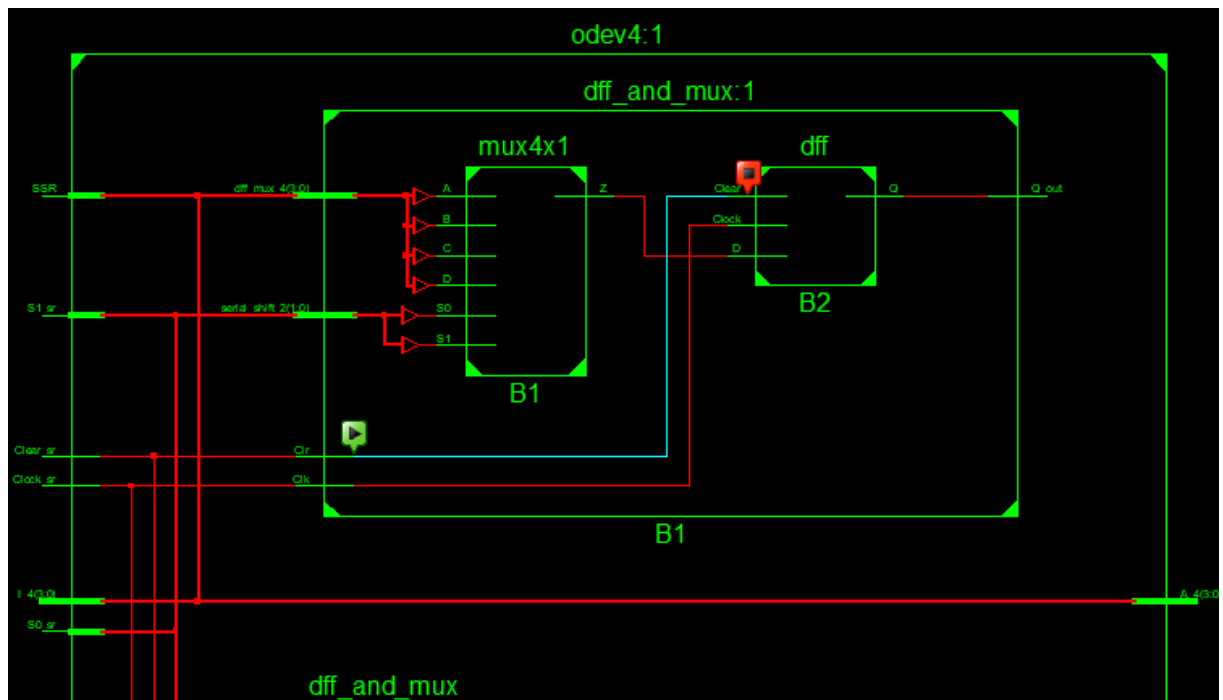

 


shift right

S ₁	S ₀	Z
0	0	A
0	1	B
1	0	C
1	1	D


shift left

rotated load


 
$$Z = \bar{S}_1 \bar{S}_0 A + \bar{S}_1 S_0 B + S_1 \bar{S}_0 C + S_1 S_0 D$$




DFF & MUX

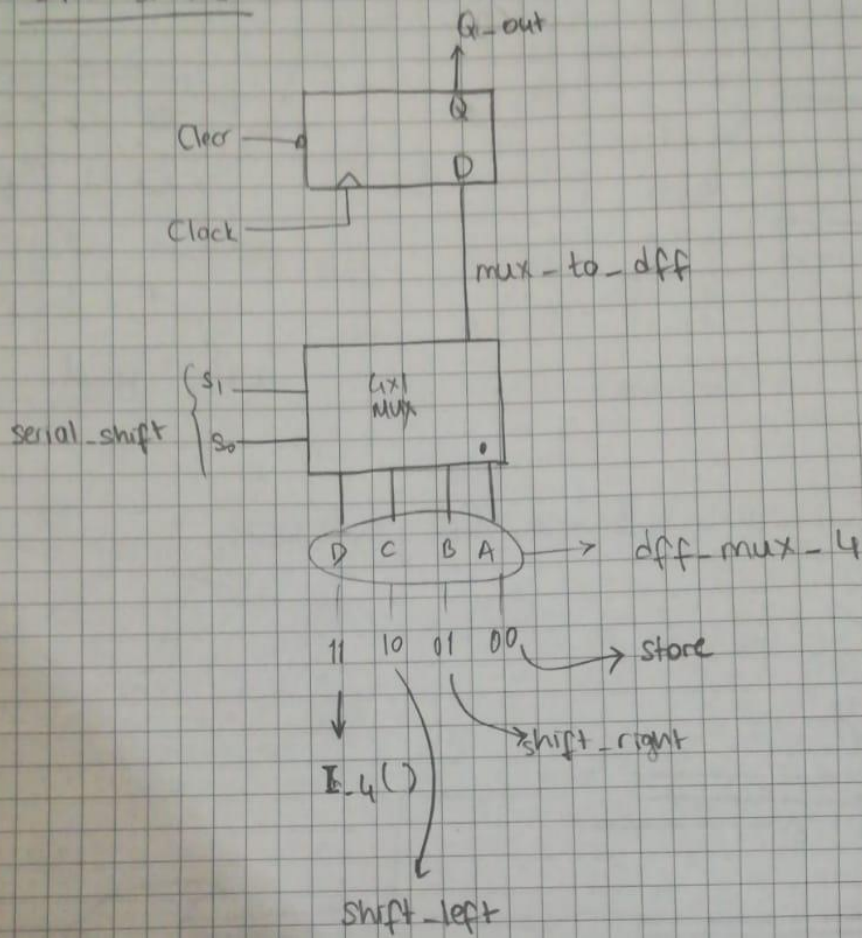


S	CLEAR	I	MSB	LSB
01	0	1010	0	1
11	1	0101	1	1
11	1	0110	1	0
10	1	1101	0	1
01	1	1111	1	1

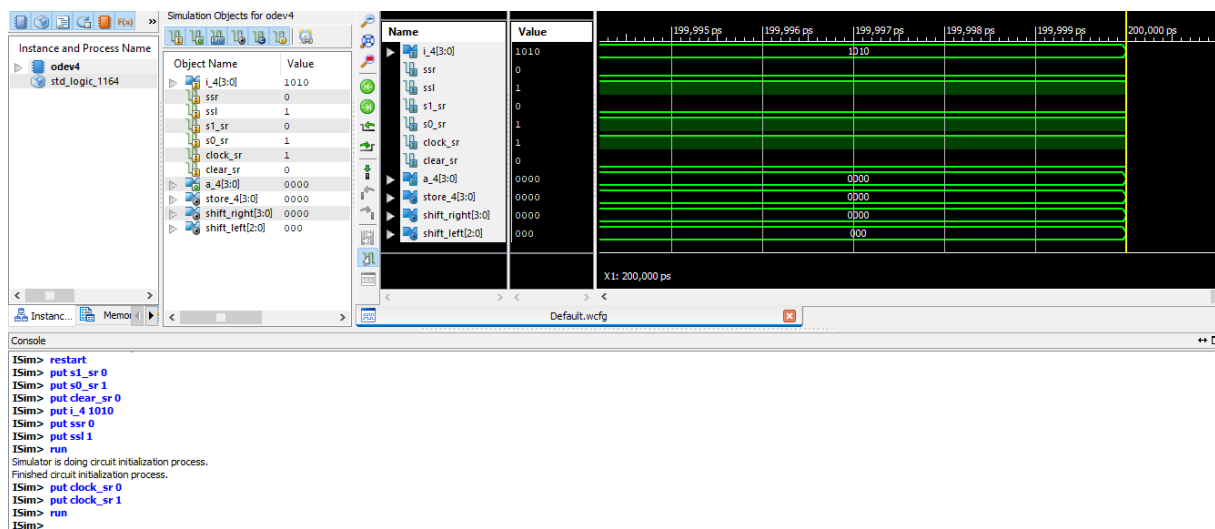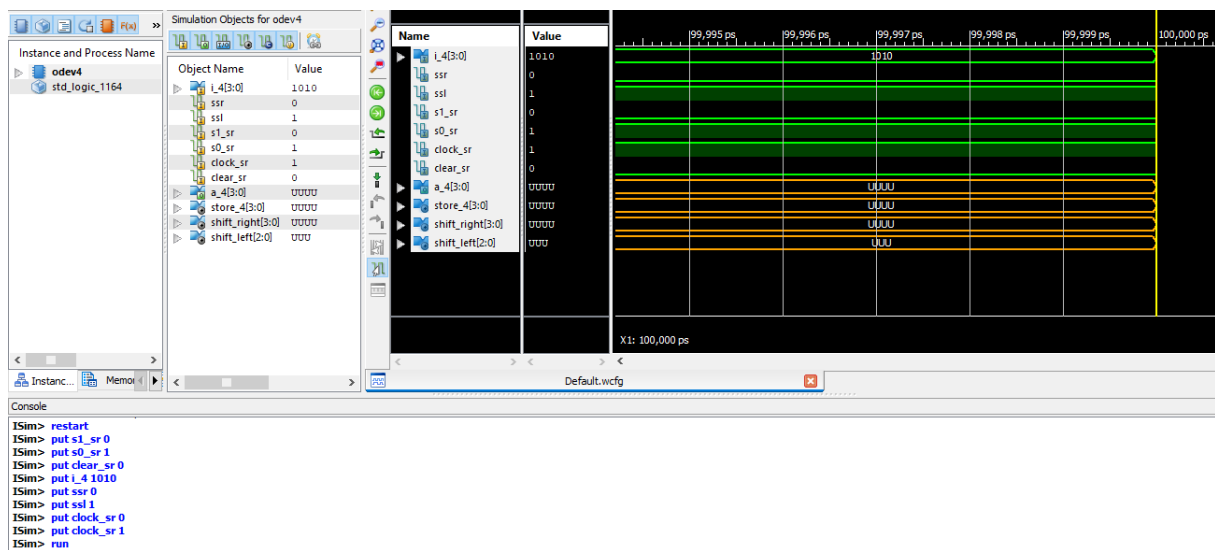


S	CLEAR	I	MSB	LSB
01	0	1010	0	1
11	1	0101	1	1
11	1	0110	1	0
10	1	1101	0	1
01	1	1111	1	1

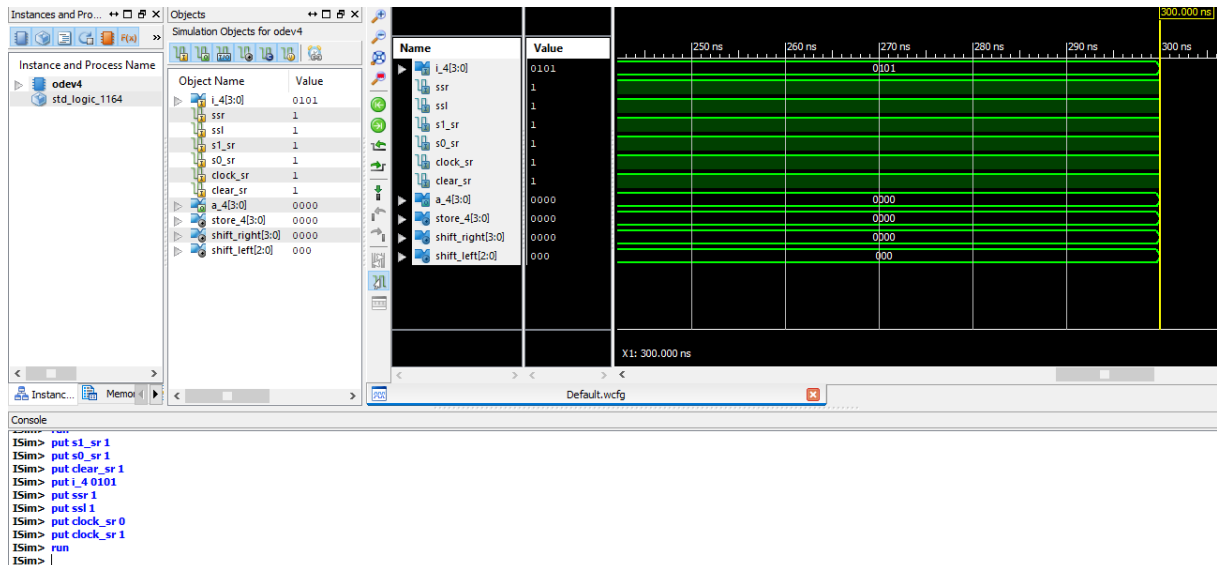

S	CLEAR	I	MSB	LSB
01	0	1010	0	1
11	1	0101	1	1
11	1	0110	1	0
10	1	1101	0	1
01	1	1111	1	1

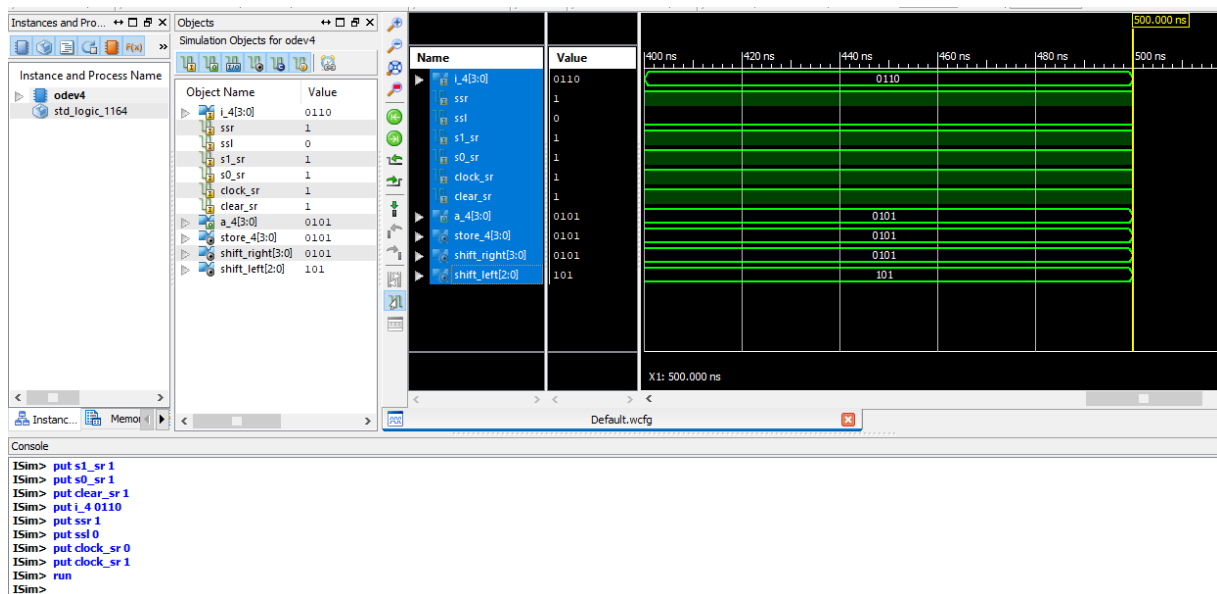

S	CLEAR	I	MSB	LSB
01	0	1010	0	1
11	1	0101	1	1
11	1	0110	1	0
10	1	1101	0	1
01	1	1111	1	1

 

S	CLEAR	I	MSB	LSB
01	0	1010	0	1
11	1	0101	1	1
11	1	0110	1	0
10	1	1101	0	1
01	1	1111	1	1

