
-- Company: İstanbul Üniversitesi - Cerrahpaşa
-- Engineer: Buse Dağıdır
--
-- Create Date: 20:37:50 11/05/2020
-- Design Name:
-- Module Name: devre - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity and_gate is

 port(and_g1: in STD_LOGIC;
 and_g2: in STD_LOGIC;
 and_x: out STD_LOGIC);

end and_gate;

architecture Behavioral of and_gate is

begin

 and_x <= and_g1 and and_g2;

end Behavioral;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity or_gate is

```
    port( or_g1, or_g2: in STD_LOGIC;  
          or_x: out STD_LOGIC);
```

end or_gate;

architecture Behavioral of or_gate is

begin

```
    or_x <= or_g1 or or_g2;
```

end Behavioral;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity dff is

```
    port( D: in STD_LOGIC;  
          Q: inout STD_LOGIC;  
          Qn: inout STD_LOGIC;  
          Clock: in STD_LOGIC;  
          Clear: in STD_LOGIC);
```

end dff;

architecture Behavioral of dff is

begin

```
    process(Clock) --eğer clock değişirse alttaki begin-end process i çalıştır --
```

```
    begin
```

```
        if(rising_edge(Clock)) then
```

```

        if(Clear='0') then
            Q <= '0';
            Qn <= '1';
        else
            Q <= D;
            Qn <= not(D);
        end if;
    end if;
end process;

```

end Behavioral;

Library IEEE;

USE IEEE.Std_logic_1164.all;

entity dff_and_or is

```

    port(    X: in STD_LOGIC;
            Clock: in STD_LOGIC;
            Z: out STD_LOGIC);

```

end dff_and_or;

architecture Behavioral of dff_and_or is

component or_gate is

```

        port( or_g1, or_g2: in STD_LOGIC;
                or_x: out STD_LOGIC);
    end component;

```

end component;

component dff is

```

    port(    Q: inout STD_LOGIC;

```

```

        Qn: inout STD_LOGIC;

        Clock: in STD_LOGIC;

        Clear: in STD_LOGIC;

        D: in STD_LOGIC);

end component;

component and_gate is
    port( and_g1: in STD_LOGIC;
          and_g2: in STD_LOGIC;
          and_x: out STD_LOGIC);

end component;


signal K: STD_LOGIC_VECTOR(5 downto 0);

begin

    B1: or_gate port map(K(0), K(1), K(2));
    B2: dff port map(K(3), K(0), Clock, '0', K(2));
    B3: and_gate port map(X, K(4), K(5));
    B4: dff port map(K(1), K(4), Clock, '0', K(5));
    B5: or_gate port map(K(3), K(5), Z);

end Behavioral;

```

 

Clock	X	Z
0	0	-
1	0	0
0	1	1
1	1	1